

Variable Supply

Basic Electronics

LM317 voltage regulator: Pinout, CALCULATOR, and circuits

By Apichet Garaipoom October 4, 2019 10 Comments

Do you need to build a variable DC power supply? It has a lot of choices for you. However, many people choose LM317 as the first, me too! Why?

Because It has high efficiency, is easy, and is cheaper.

It can replace 1.5 V or 9 V battery and others *as we want to do*.

Is it really? You find out below.

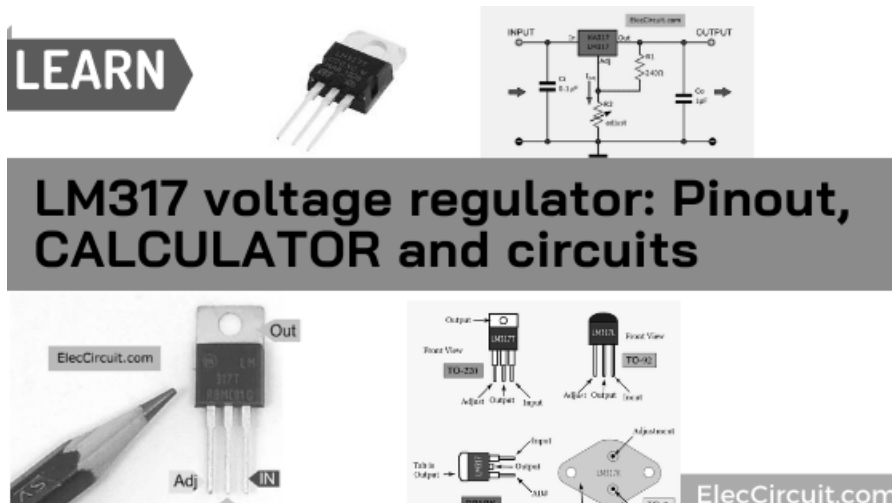


Table of Contents [hide]

LM317 Datasheet

LM317 pinout

Basic Features

LM317 calculator

Output Voltage with R1 and R2 List

LM317 heat sink calculator

For example LM317 circuit

LM317 Datasheet

It is an adjustable 3-terminal positive voltage regulator, to supply more than 1.5 A of load current, and an output adjustable voltage: 1.2 V to 37 V range.

Also, LM317 has an internal current limiting, temperature detects shutdown and safe area compensation.

LM317 pinout


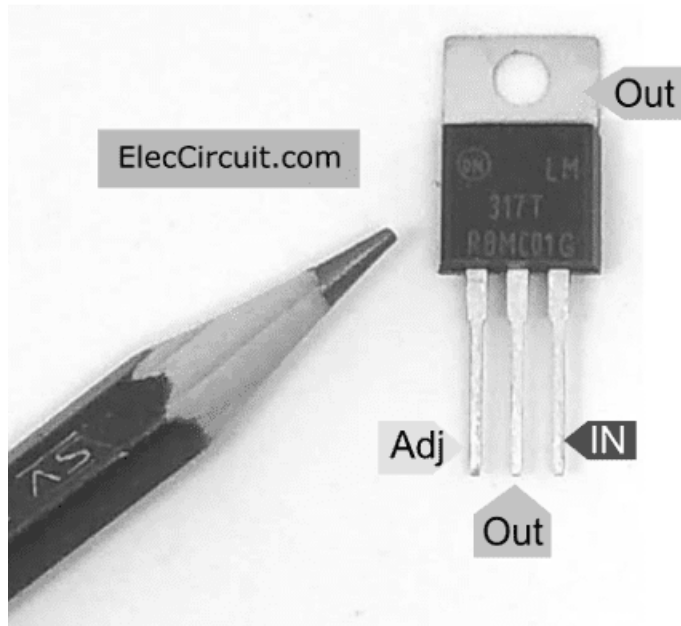


Figure 1: LM317 pinout on TO-220

Look:

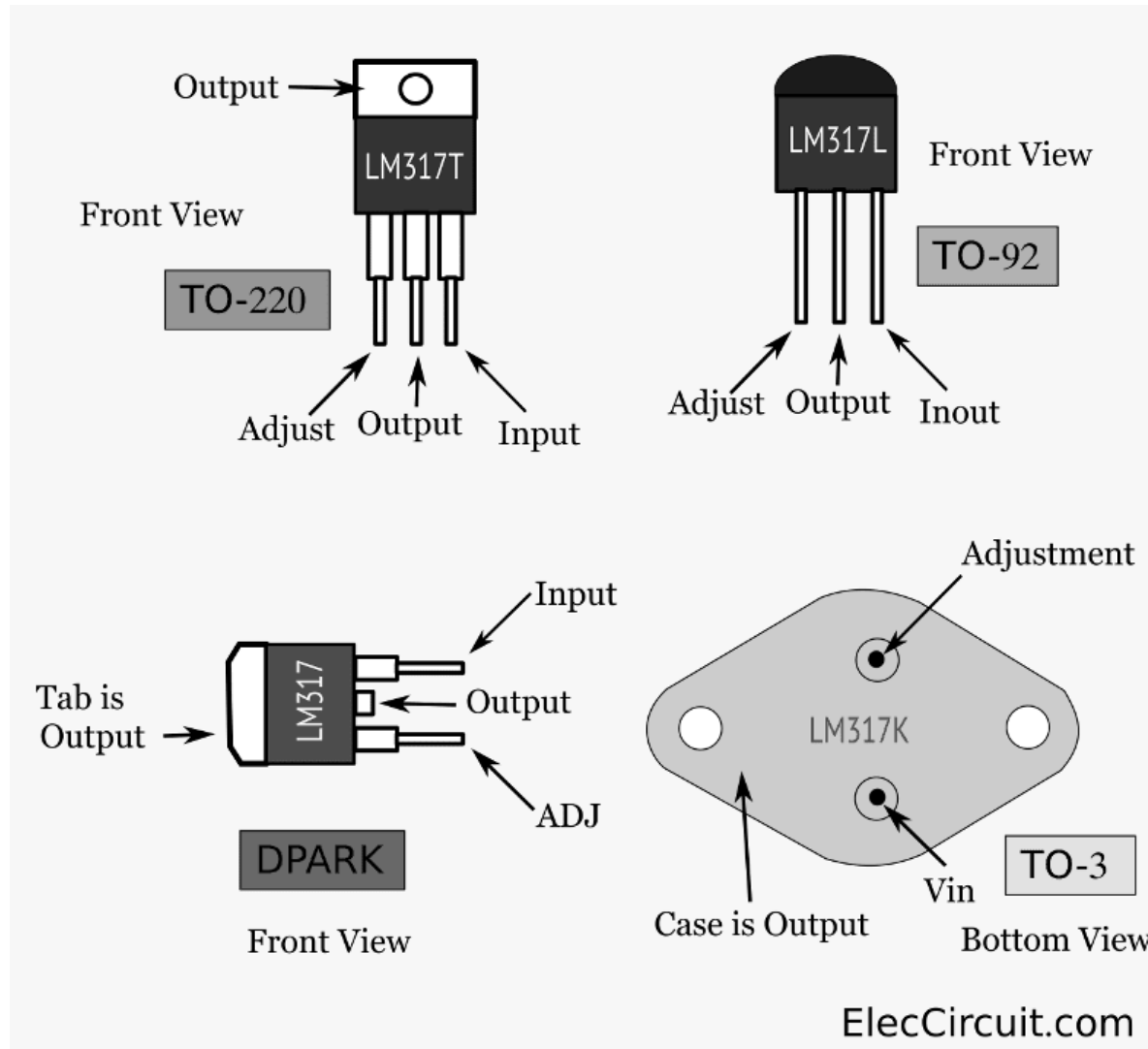

Connection Diagram various LM317 Pinout

- LM317T on TO-220: output 1.5 A

- LM317K on TO-3: output 1.5 A
- LM317 on DPARK: output 1.5 A

Basic Features

- Output current in excess of 1.5 A
- Output-Adjustable between 1.2 V to 37 V
- Internal Short-Circuit Current Limiting or Output is short-circuit protected
- Internal Thermal Overload Protection or Current limit constant with temperature
- Output-Transistor Safe Operating Area Compensation
- TO-220 Package like 2SC1061 transistors.
- There are 1% output voltage Durability
- There are max. 0.01% / V line regulation(LM317), and 0.3% load regulation (LM117)
- There are 80 dB ripple rejection

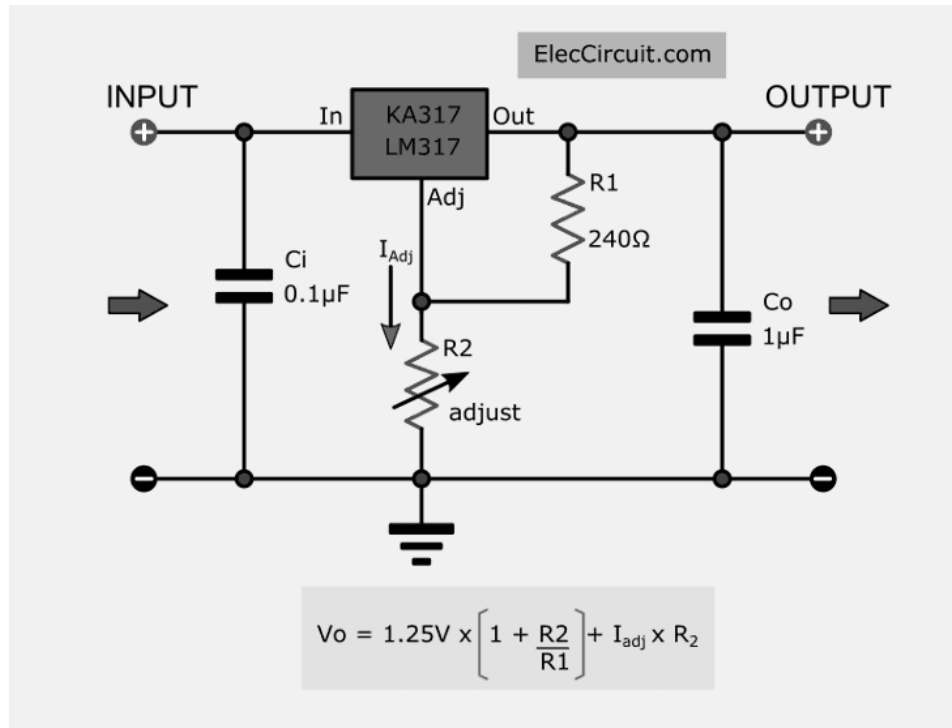


Figure 2 the basic circuit diagram

Basic circuit diagram

If the distance from the IC regulator and input voltage is too much. We should put C_i to reduce any noise.

Next, see the figure circuit. You not need to put C_o . But You want a high-efficiency output. You should add It to keep lower an ripple.

As I_{Adj} is controlled to less than 100 μA , the little error is unimportant in most uses.

Learn more: [IC Voltage Regulators Information](#)

LM317 calculator

This **calculator** will work for most DC Voltage Regulators with a reference voltage (V_{REF}) of 1.25. Typically, the program resistor ($R1$) is 240 ohms for the LM117, LM317, LM138, and LM150.

Some said I_{adj} is very low current.

So, we may reduce it down. To be shorter and easy.

$$V_{out} = 1.25 \text{ V} \times \{1 + R2 / R1\}$$

Which is better?

For example:

You use $R1 = 270 \text{ ohms}$ and $R2 = 390 \text{ ohms}$. It causes output is 3.06 V

Is it easy? If you have voltages choice with most resistors. In local stores near you.

look at the list:

Output Voltage with R1 and R2 List

1.43V : $R1 = 470\Omega$, $R2 = 68\Omega$

1.47V : $R1 = 470\Omega$, $R2 = 82\Omega$

1.47V : $R1 = 390\Omega$, $R2 = 68\Omega$

1.51V : R1 = 390Ω, R2 = 82Ω

1.52V : R1 = 470Ω, R2 = 100Ω

1.53V : R1 = 390Ω, R2 = 82Ω

1.56V : R1 = 330Ω, R2 = 82Ω

1.57V : R1 = 270Ω, R2 = 68Ω

1.57V : R1 = 470Ω, R2 = 120Ω

1.57V : R1 = 390Ω, R2 = 100Ω

1.59V : R1 = 390Ω, R2 = 100Ω

1.60V : R1 = 240Ω, R2 = 68Ω

1.63V : R1 = 330Ω, R2 = 100Ω

1.63V : R1 = 270Ω, R2 = 82Ω

1.64V : R1 = 390Ω, R2 = 120Ω

1.64V : R1 = 220Ω, R2 = 68Ω

1.65V : R1 = 470Ω, R2 = 150Ω

1.66V : R1 = 390Ω, R2 = 120Ω

1.68V : R1 = 240Ω, R2 = 82Ω

1.71V : R1 = 330Ω, R2 = 120Ω

1.71V : R1 = 270Ω, R2 = 100Ω

1.72V : R1 = 220Ω, R2 = 82Ω

1.72V : R1 = 180Ω, R2 = 68Ω

1.73V : R1 = 470Ω, R2 = 180Ω

1.73V : R1 = 390Ω, R2 = 150Ω

1.76V : R1 = 390Ω, R2 = 150Ω

1.77V : R1 = 240Ω, R2 = 100Ω

1.81V : R1 = 270Ω, R2 = 120Ω

1.82V : R1 = 150Ω, R2 = 68Ω

1.82V : R1 = 330Ω, R2 = 150Ω

1.82V : R1 = 180Ω, R2 = 82Ω

1.83V : R1 = 390Ω, R2 = 180Ω

1.86V : R1 = 390Ω, R2 = 180Ω

1.88V : R1 = 240Ω, R2 = 120Ω

1.89V : R1 = 470Ω, R2 = 240Ω

1.93V : R1 = 330Ω, R2 = 180Ω

1.93V : R1 = 150Ω, R2 = 82Ω

1.94V : R1 = 270Ω, R2 = 150Ω

1.96V : R1 = 390Ω, R2 = 220Ω

1.97V : R1 = 470Ω, R2 = 270Ω

1.99V : R1 = 390Ω, R2 = 220Ω

2.02V : R1 = 390Ω, R2 = 240Ω

2.03V : R1 = 240Ω, R2 = 150Ω

2.06V : R1 = 390Ω, R2 = 240Ω

2.08V : R1 = 330Ω, R2 = 220Ω

2.10V : R1 = 220Ω, R2 = 150Ω

2.12V : R1 = 390Ω, R2 = 270Ω

2.13V : R1 = 470Ω, R2 = 330Ω

2.16V : R1 = 330Ω, R2 = 240Ω

2.16V : R1 = 390Ω, R2 = 270Ω

2.19V : R1 = 240Ω, R2 = 180Ω

2.23V : R1 = 470Ω, R2 = 390Ω

2.25V : R1 = 150Ω, R2 = 120Ω

2.27V : R1 = 270Ω, R2 = 220Ω

2.27V : R1 = 330Ω, R2 = 270Ω

2.29V : R1 = 470Ω, R2 = 390Ω

2.29V : R1 = 180Ω, R2 = 150Ω

2.31V : R1 = 390Ω, R2 = 330Ω

2.36V : R1 = 270Ω, R2 = 240Ω

2.37V : R1 = 390Ω, R2 = 330Ω

2.44V : R1 = 390Ω, R2 = 390Ω

2.50V : R1 = 470Ω, R2 = 470Ω

2.57V : R1 = 390Ω, R2 = 390Ω

2.61V : R1 = 220Ω, R2 = 240Ω

2.65V : R1 = 330Ω, R2 = 390Ω

2.66V : R1 = 240Ω, R2 = 270Ω

2.73V : R1 = 330Ω, R2 = 390Ω

2.74V : R1 = 470Ω, R2 = 560Ω

2.75V : R1 = 150Ω, R2 = 180Ω

2.76V : R1 = 390Ω, R2 = 470Ω

2.78V : R1 = 270Ω, R2 = 330Ω

2.78V : R1 = 220Ω, R2 = 270Ω

2.84V : R1 = 390Ω, R2 = 470Ω

2.92V : R1 = 180Ω, R2 = 240Ω

2.96V : R1 = 270Ω, R2 = 390Ω

2.97V : R1 = 240Ω, R2 = 330Ω

3.03V : R1 = 330Ω, R2 = 470Ω

3.05V : R1 = 390Ω, R2 = 560Ω

3.06V : R1 = 270Ω, R2 = 390Ω

3.06V : R1 = 470Ω, R2 = 680Ω

3.08V : R1 = 150Ω, R2 = 220Ω

3.13V : R1 = 220Ω, R2 = 330Ω

3.14V : R1 = 390Ω, R2 = 560Ω

3.18V : R1 = 240Ω, R2 = 390Ω

3.25V : R1 = 150Ω, R2 = 240Ω

3.28V : R1 = 240Ω, R2 = 390Ω

3.35V : R1 = 220Ω, R2 = 390Ω

3.37V : R1 = 330Ω, R2 = 560Ω

3.43V : R1 = 390Ω, R2 = 680Ω

3.43V : R1 = 470Ω, R2 = 820Ω

3.47V : R1 = 220Ω, R2 = 390Ω

3.50V : R1 = 150Ω, R2 = 270Ω

3.54V : R1 = 180Ω, R2 = 330Ω

3.55V : R1 = 390Ω, R2 = 680Ω

3.70V : R1 = 240Ω, R2 = 470Ω

3.82V : R1 = 180Ω, R2 = 390Ω

3.83V : R1 = 330Ω, R2 = 680Ω

3.84V : R1 = 270Ω, R2 = 560Ω

3.88V : R1 = 390Ω, R2 = 820Ω

3.91V : R1 = 470Ω, R2 = 1K

3.92V : R1 = 220Ω, R2 = 470Ω

3.96V : R1 = 180Ω, R2 = 390Ω

4.00V : R1 = 150Ω, R2 = 330Ω

4.02V : R1 = 390Ω, R2 = 820Ω

4.17V : R1 = 240Ω, R2 = 560Ω

4.33V : R1 = 150Ω, R2 = 390Ω

4.36V : R1 = 330Ω, R2 = 820Ω

4.40V : R1 = 270Ω, R2 = 680Ω

4.43V : R1 = 220Ω, R2 = 560Ω

4.44V : R1 = 470Ω, R2 = 1.2K

4.46V : R1 = 390Ω, R2 = 1K

4.50V : R1 = 150Ω, R2 = 390Ω

4.51V : R1 = 180Ω, R2 = 470Ω

4.63V : R1 = 390Ω, R2 = 1K

4.79V : R1 = 240Ω, R2 = 680Ω

5.04V : R1 = 330Ω, R2 = 1K

5.10V : R1 = 390Ω, R2 = 1.2K

5.11V : R1 = 220Ω, R2 = 680Ω

5.14V : R1 = 180Ω, R2 = 560Ω

5.17V : R1 = 150Ω, R2 = 470Ω

5.24V : R1 = 470Ω, R2 = 1.5K

5.30V : R1 = 390Ω, R2 = 1.2K

5.52V : R1 = 240Ω, R2 = 820Ω

5.80V : R1 = 330Ω, R2 = 1.2K

5.88V : R1 = 270Ω, R2 = 1K

5.91V : R1 = 220Ω, R2 = 820Ω

5.92V : R1 = 150Ω, R2 = 560Ω

5.97V : R1 = 180Ω, R2 = 680Ω

6.04V : R1 = 470Ω, R2 = 1.8K

6.06V : R1 = 390Ω, R2 = 1.5K

6.32V : R1 = 390Ω, R2 = 1.5K

6.46V : R1 = 240Ω, R2 = 1K

6.81V : R1 = 270Ω, R2 = 1.2K

6.92V : R1 = 150Ω, R2 = 680Ω

6.93V : R1 = 330Ω, R2 = 1.5K

6.94V : R1 = 180Ω, R2 = 820Ω

7.02V : R1 = 390Ω, R2 = 1.8K

7.10V : R1 = 470Ω, R2 = 2.2K

7.33V : R1 = 390Ω, R2 = 1.8K

7.50V : R1 = 240Ω, R2 = 1.2K

8.07V : R1 = 330Ω, R2 = 1.8K

8.08V : R1 = 150Ω, R2 = 820Ω

8.19V : R1 = 270Ω, R2 = 1.5K

8.30V : R1 = 390Ω, R2 = 2.2K

8.68V : R1 = 390Ω, R2 = 2.2K

9.06V : R1 = 240Ω, R2 = 1.5K

9.58V : R1 = 330Ω, R2 = 2.2K

9.77V : R1 = 220Ω, R2 = 1.5K

9.90V : R1 = 390Ω, R2 = 2.7K

10.03V : R1 = 470Ω, R2 = 3.3K

10.37V : R1 = 390Ω, R2 = 2.7K

10.63V : R1 = 240Ω, R2 = 1.8K

11.25V : R1 = 150Ω, R2 = 1.2K

11.44V : R1 = 270Ω, R2 = 2.2K

11.48V : R1 = 330Ω, R2 = 2.7K

11.67V : R1 = 180Ω, R2 = 1.5K

11.83V : R1 = 390Ω, R2 = 3.3K

12.40V : R1 = 390Ω, R2 = 3.3K

12.71V : R1 = 240Ω, R2 = 2.2K

13.75V : R1 = 330Ω, R2 = 3.3K

15.31V : R1 = 240Ω, R2 = 2.7K

16.25V : R1 = 150Ω, R2 = 1.8K

16.53V : R1 = 270Ω, R2 = 3.3K

16.59V : R1 = 220Ω, R2 = 2.7K

18.44V : R1 = 240Ω, R2 = 3.3K

19.58V : R1 = 150Ω, R2 = 2.2K

20.00V : R1 = 220Ω, R2 = 3.3K

23.75V : R1 = 150Ω, R2 = 2.7K

24.17V : R1 = 180Ω, R2 = 3.3K

28.75V : R1 = 150Ω, R2 = 3.3K

For example:

How to do it?

You have only LM317 and a lot of resistors. Yes! you can use them instead.

Look at the list above, in 4.5V voltage. We can use $R1 = 150\Omega$, $R2 = 390\Omega$.

It is easy, right?

LM317 heat sink calculator

What is the size of the heat sink enough?

LM317 is always hot while working. Though it has an over-temperature cut-out mode. But we should not release it too hot. We always install the heat sink.

Someone ask me. What size heat sink should we use? LM317 has a maximum temperature of $50\text{ }^{\circ}\text{C/W}$ without a heat sink.

I found this site, good for using LM317 heat sink calculator.

The LM317 Heat sink, how big?

You can find *the LM317* on Amazon [here](#) if you're interested.

For example LM317 circuit

1. First Variable DC Power Supply

I built it as a first power supply. Though it is very old, we have still used them for more than 20 years. Why it is great like this?

2. Linear Selector Power supply Regulator

Easy to select the output voltage: 1.5V, 3V, 4.5V, 5V, 6V, 9V at 1.5A

3. 30V Dual DC variable power supply

High voltage 0V to 60 volts at 1.5A and starts voltage at zero! good job.

4. Great DC power supply

High quality, 3A adjustable voltage regulator. Using LM317 and 2N3055 so easy and cheap. Adjust voltage in steps 3V, 6V, 9V, 12V. And in fine, 1.25V to 20V.

5. 4 Lead Acid Battery charger circuits

See 4 LM317 Lead-acid battery charger circuits for 6V, 12V, and 24V battery. With automatic charging and full charged Indicator using TL431. Easy to build.

6. Dual power supply 3V,5V,6V,9V,12,15V

Dual power supply circuit, can select voltage levels 3V, 5V, 6V, 9V, 12V, 15V at 1A and -3V, -5V, -6V, -9V, -12V, -15V at 1A, use LM317 (positive) LM337 (negative) [...]

7. USB Battery Replacement

This is a USB 5V to 1.5V Step-Down Converter Circuit. When we use a Cheap MP3 Player which uses only one 1.5V AA battery as its power supply.

8. Low dropout 5v regulator

This is 5V low dropout regulator circuit using a transistor and LED only so easy, lowest

9. Gel cell battery charger circuit

It can charge any size of the Gel cell batteries and extend the life of the Gel Cell battery. While the circuit is running, the LED indicates charging.

10. Nicad Battery Charger using LM317T

Here are Universal NiCd and NiMH battery charger circuit. It uses IC LM317T (Hot IC) Control Current less 300mA, Size battery 2.4V,4.8V,9.6V. Low-cost circuit

GET UPDATE VIA EMAIL

I always try to make Electronics **Learning Easy**.

Subscribe

Last updated on December 2, 2021

Apichet Garaipoom

I love electronic circuits. I will collect a lot of circuit electronics to teach my son and are useful for everyone. Thanks for your support.

10 Comments

worku

Reply

January 26, 2016, 6:17 am

Thank's & GBU this EC member .

vishal

Reply

February 2, 2016, 8:22 pm

sir i want 5v,2a power supply circuit with calculation from 230

sunday owen

Reply

June 12, 2016, 10:53 pm

pleasr can this idea be used to build solar charge controller?

Sumithra

Reply

July 20, 2016, 3:37 am

Pls suggest any simple circuit which supplies output of +12V , -12V dual output with current rating of 1A

I/p supply is +24V DC .

IAM LEANING A LOT I THANK VERY MUCH OUT OF THE MANY THINGS
U ARE REVIEWING.

Abiodun Ogundipe

Reply

August 4, 2017, 10:26 am

Dear Sir/Ma

We are spare part supplier in Nigeria,

Company name with address

DE- ACCORD SYNERGY CONCEPT NIG LIMiTED. NO6, Oba Amusa

Avenue Sumbol Bus Stop, Lagos Nigeria.

Kindly quote us for the bellow items for our customer.

LM78S40 (Universal Switching Regulator) 2nos

LM7805 (Voltage Regulator) 2nos

Your best price and delivery

Best Regards

Abiodun Ogundipe

+23435766398

KUMERASAN

Reply

July 1, 2020, 4:45 am

halogen bulb

input voltage is 12v AC and out put 6v dc with variable pot using matal cap transistor like LM317K.

A **Apichet Garaipoom**

Reply

August 12, 2020, 8:20 pm

Hello, Kumerasan

Thanks for visiting.

It is a good idea. Let me give you a comment. What is the small halogen rate, current or watts? Here is 5watts <https://amzn.to/2XTskJm>
It uses current about $5W/6V = 0.8A$. Yes, you can use LM317. It may very heat. But if you use 10W. It will use current more = $10w/6V = 1.6A$.

You cannot use alone LM317. You may use it with a power transistor. Or use LM350. It is easy, too. <https://www.eleccircuit.com/lm350-adjustable-voltage-regulator/>

I hope this can help you.

Ps. I also had the idea of using hydrogen tubes for my chickens.

Do have chickens?

m0n0

Reply

November 15, 2021, 8:49 am

ortographic sense...

A **Apichet Garaipoom**

Reply

December 30, 2021, 10:03 am

Hello m0n0,

Thanks for your opinion. I will try to improve my English. I hope you will read this article again.

Thanks a lot again my friends.

This site uses Akismet to reduce spam. [Learn how your comment data is processed.](#)